

21 Jan 2016

A Cockcroft-Walton HV-Generator / PMT-Base for NPS

Joshua Frechem

Charles Hyde

Old Dominion University

Why C-W Base?


- No HV cables – cuts cost
- Less (?) power dissipation.
- Better (?) stability vs pile-up fluctuations.
- Design Example:
 - ZEUS HCal → JLab/IU Rad Φ → RHIC AnDY

Cockcroft-Walton Concept

- Generate HV with a DC Transformer
 - High frequency pulse generator drives a capacitor/diode ladder
 - Rectifiers stacked on rectifiers
 - Our version, $0 \rightarrow +5V$ pulse at 10–40 KHz drives a transformer to $\sim 100V$
 - Transformer drives ~ 20 stage ladder


GND

Photocathode end

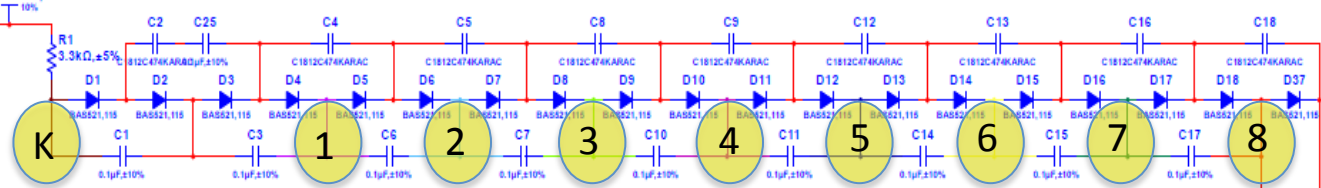

Dynodes

Anode/Ground end

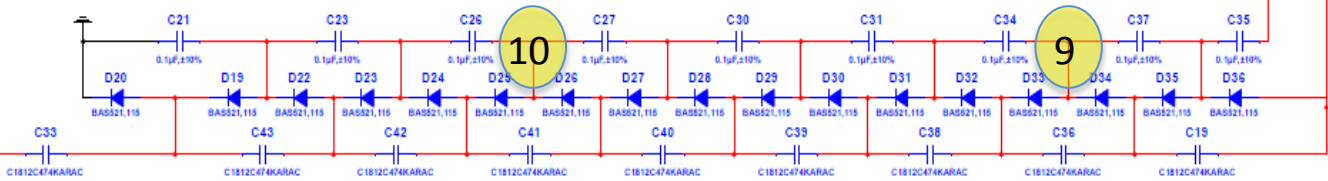

Pulse to CW

Feedback to ADC

+12

-12


USB

Arduino nano

On/Off Switch


Comm to DAC


HVenable


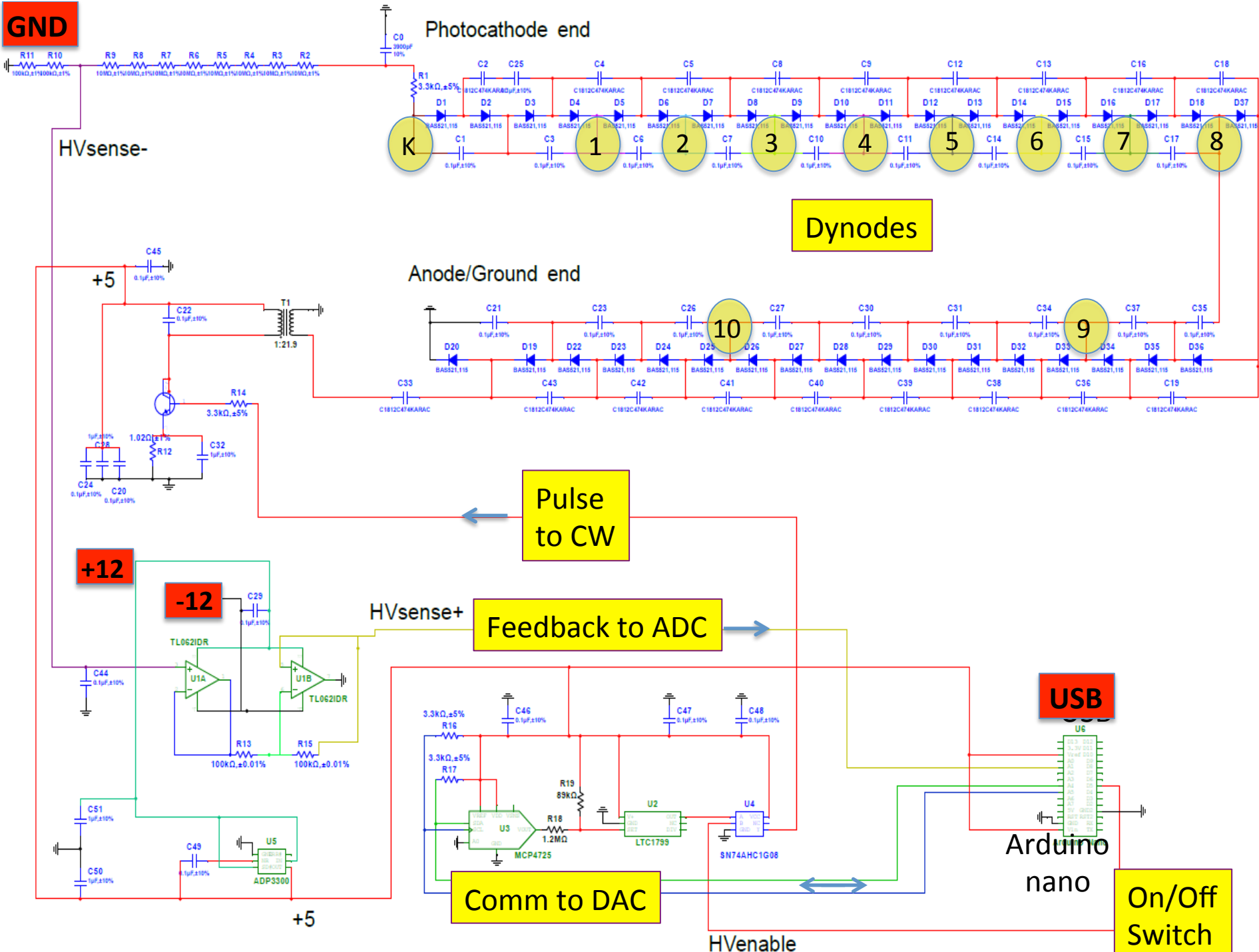


Benefits of Using Arduino

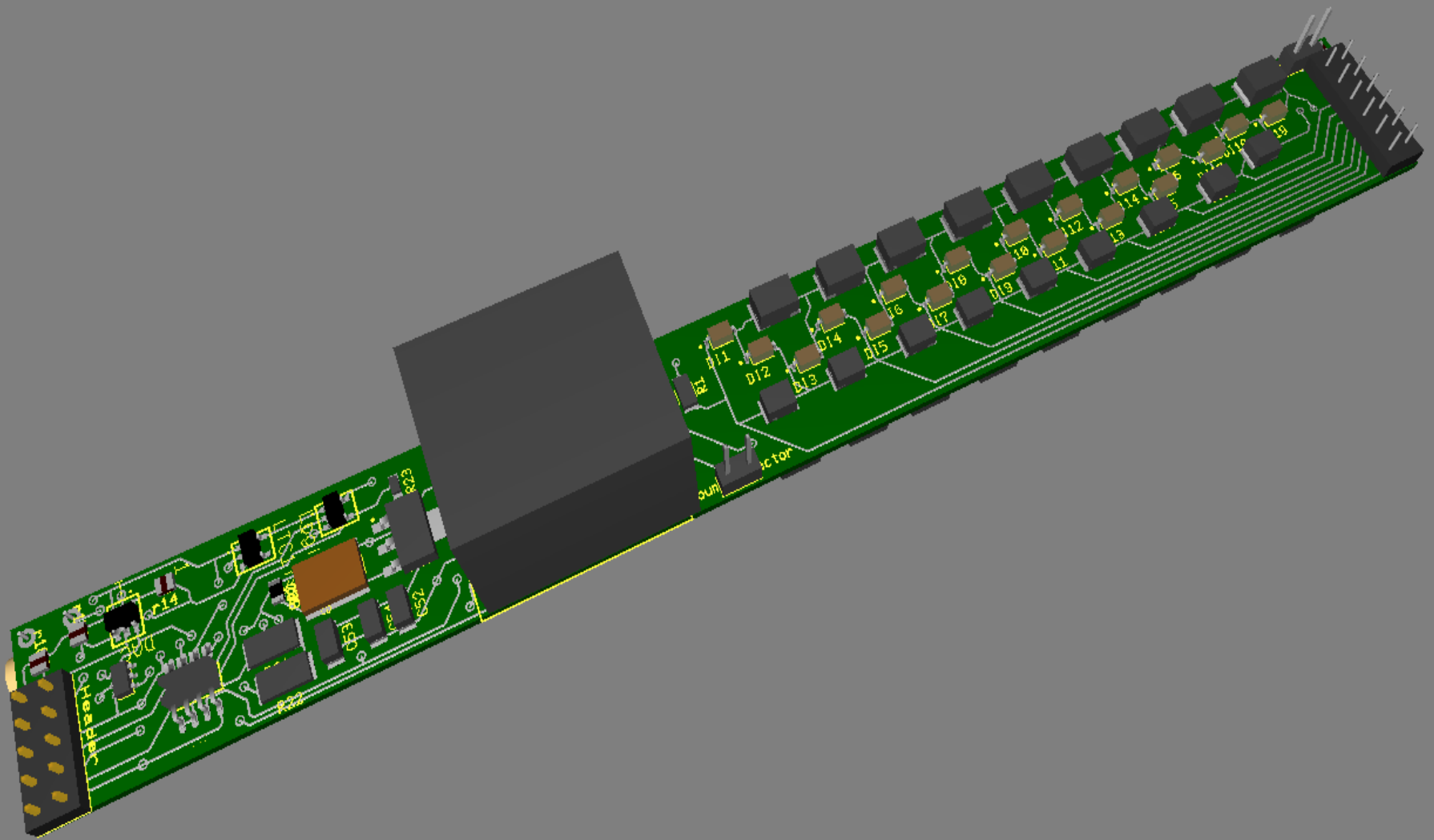
- Easily programmable through the IDE vs ISP
 - This can be done remotely while installed via USB
- Scripts can be written to sequentially program
 - Eliminates manually having to upload code to each board
- Programs can be used/written to monitor & save
 - Save and monitor HV level for stability
- Easily turn HV on/off via logic gate



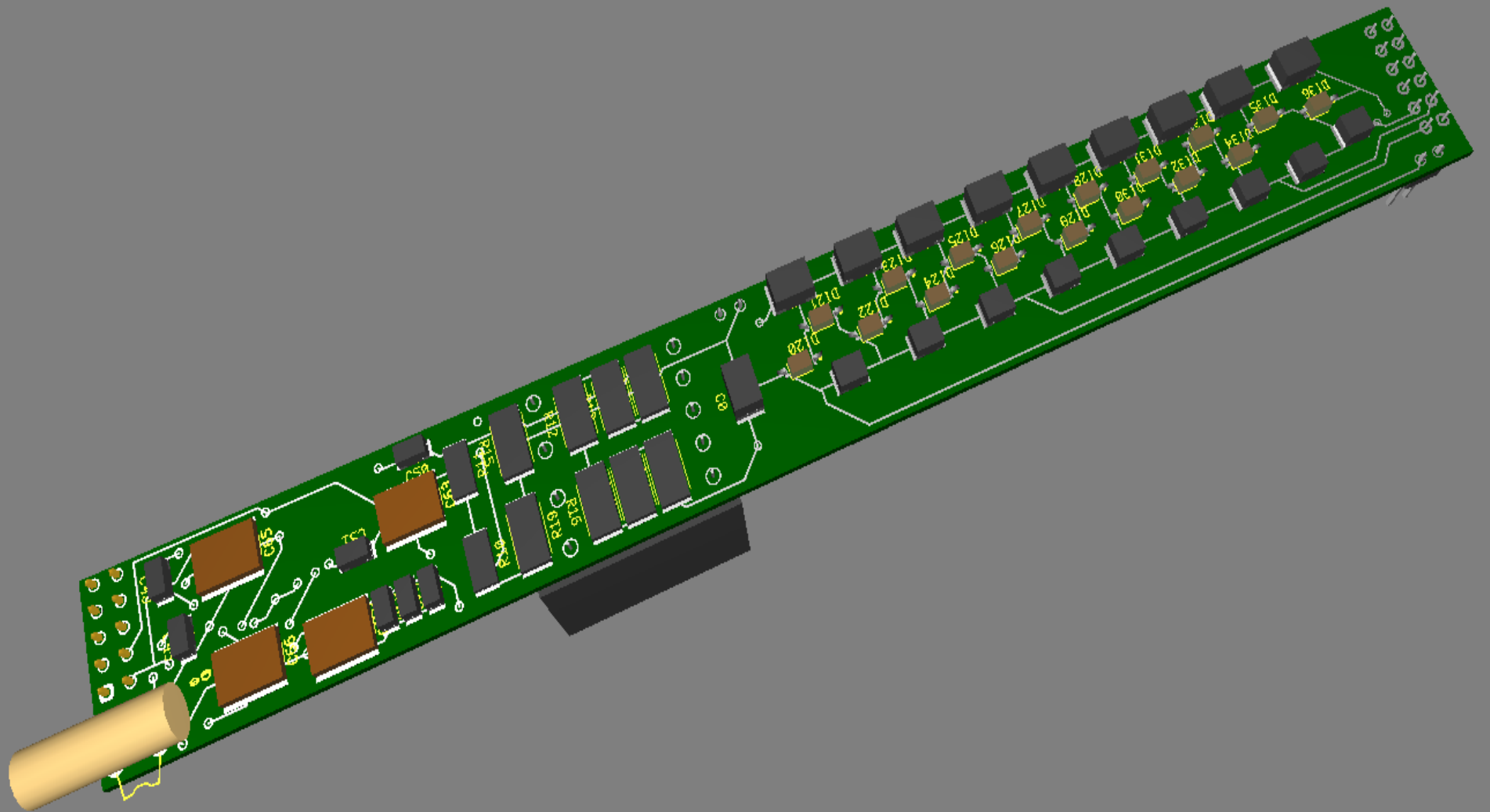


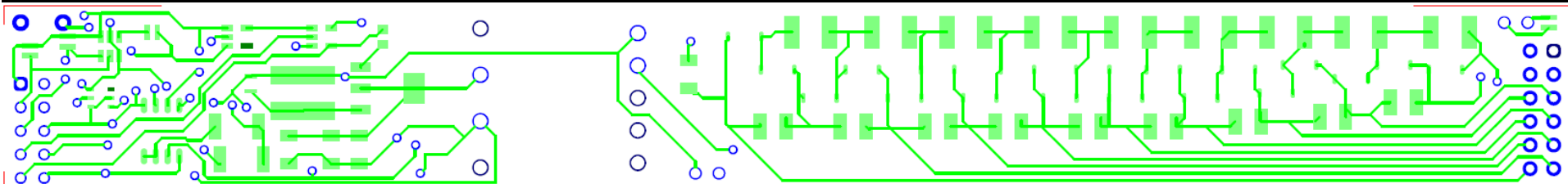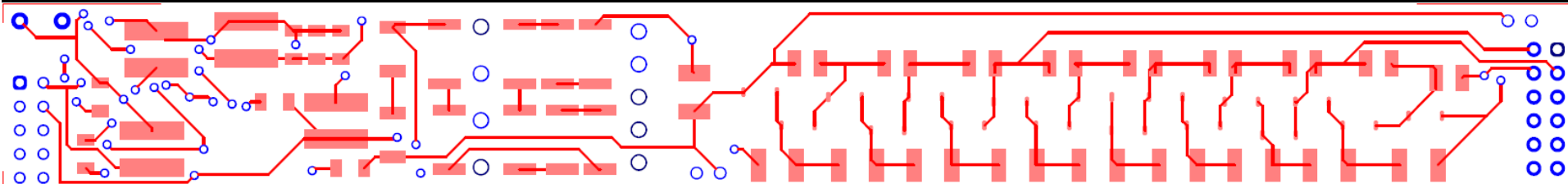

Readback is linear

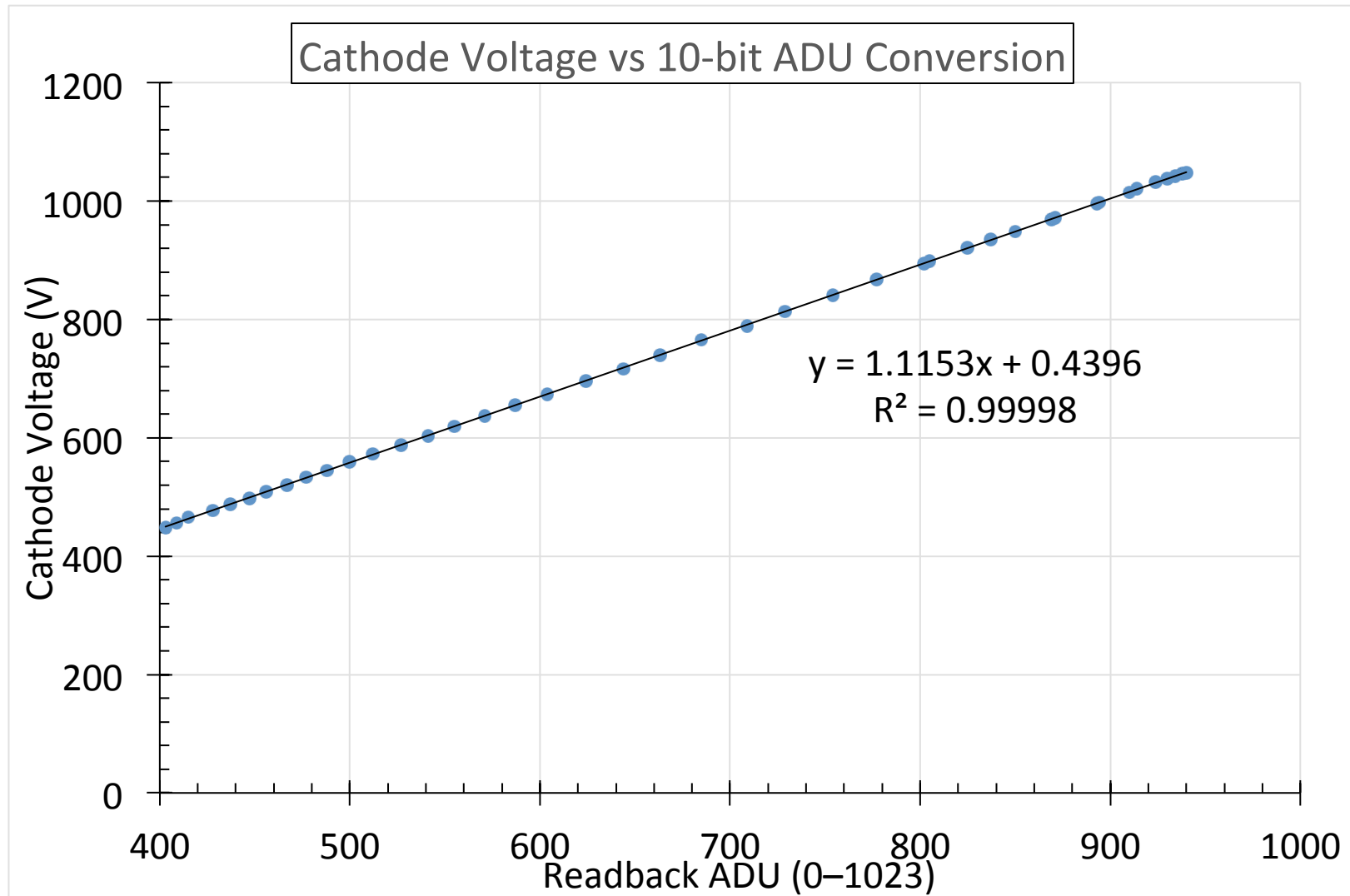


Affect of Resonance on Feedback

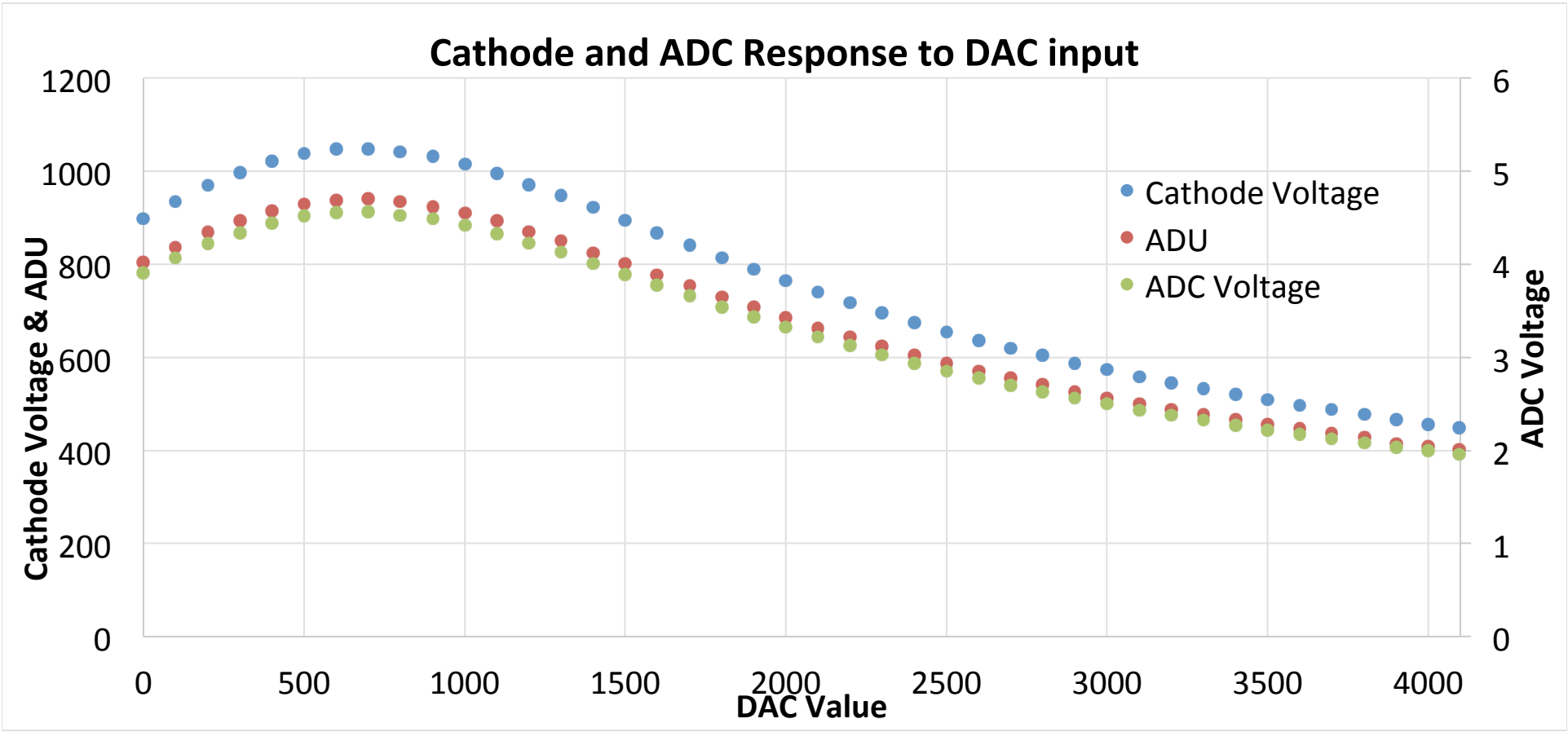

Effect of Resonance on Feedback

- Frequency range can be set to exclude resonance
 - Change resistance between Vcc & Set on oscillator
 - Easier control for when $V_{set} < V_{resonance}$
- Creates a non-linearity that is compensated for in code
- Create code so that resonance frequency is not reached

Sample HV Signal: It Works!

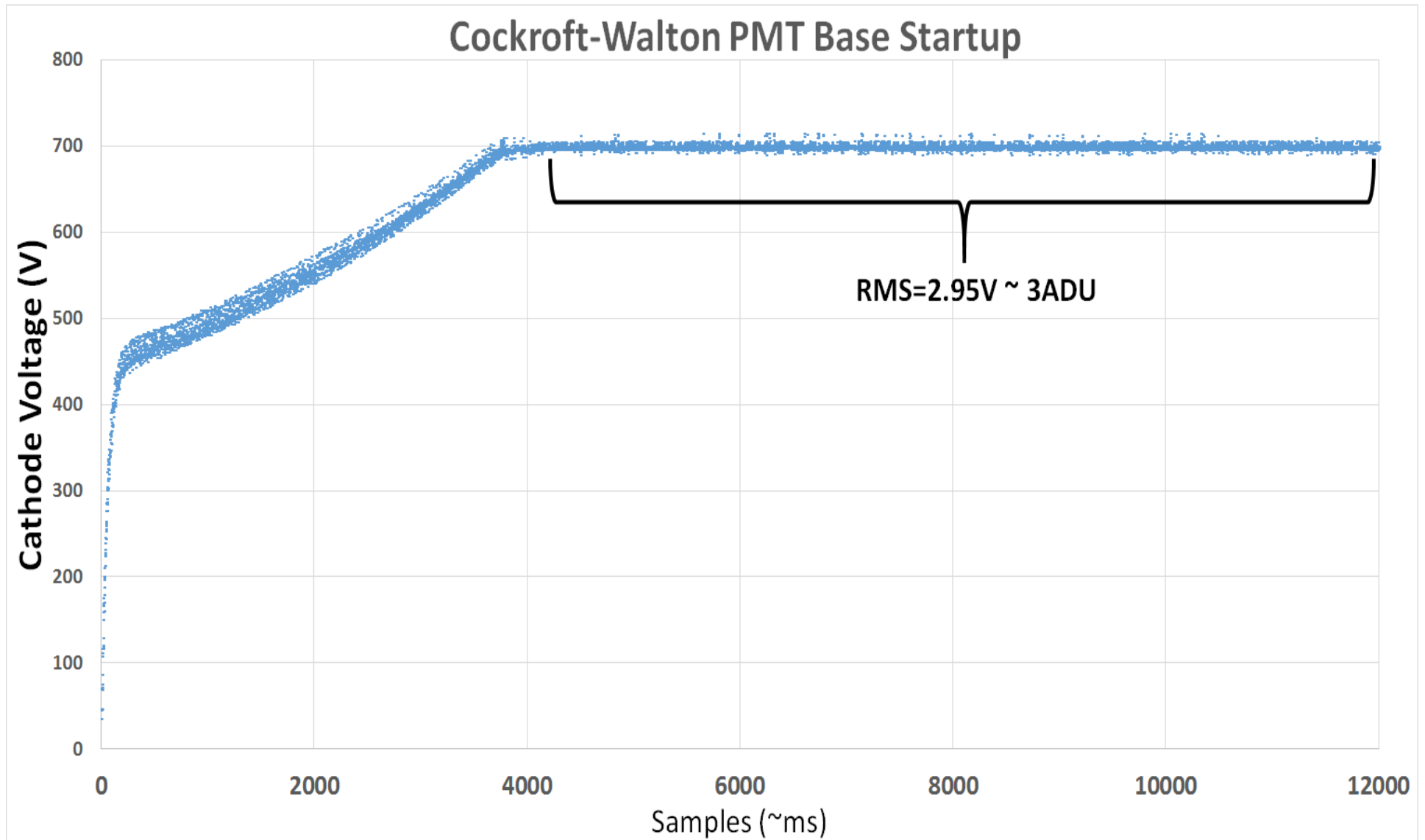

Planned Additions

- Mount Arduino on to PCB
- 12bit ADC separate from MCU
 - Allows finer control to match 12bit DAC
- Additional ADP3300 voltage regulator
 - Lower noise supply powering Arduino & transformer
- Smaller transformer
 - Isolation transformer to separate HV chain from digital components?

Cost Per Board @1000

Mfr. #	Manufacturer	Desc.	Order Qty.	Price (USD)	Ext.: (USD)
PZT3904	Fairchild Semiconductor	BJT NPN Transistor General Purpose	1000	\$0.108	\$108.00
750871011	Würth Electronics	Transformers Audio & Signal 4mH 1.60Ohm	1000	\$5.41	\$5,410.00
MCP4725A0T-E/CH	Microchip	Digital to Analog Converters - DAC Sngl 12B NV DAC	1000	\$0.73	\$730.00
SN74AHC1G08DBVR	Texas Instruments	Logic Gates Single 2-Input	1000	\$0.103	\$103.00
ADP3300ARTZ-5REEL7	Analog Devices Inc.	Linear Voltage Regulators High Acc 50mA LDO	1000	\$0.666	\$666.00
TL062IDR	Texas Instruments	Op Amps Dual Low-Noise JFET-Input	1000	\$0.282	\$282.00
CRCW080533R0FKEA	Vishay	1/8watt 33ohms 1% 100ppm	1000	\$0.019	\$19.00
ERJ-P08J332V	Panasonic	1206 3300ohms 5% Thick Film Resistor	5000	\$0.017	\$85.00
ERJ-3EKF8872V	Panasonic	0603 88.7Kohms 1% Tol	1000	\$0.004	\$4.00
CRCW2010100KFKEF	Vishay	3/4watt 100Kohms 1%	3000	\$0.07	\$210.00
1812HC392KAT1A	AVX	3900 pF 10% 3 KVolts X7R	1000	\$0.384	\$384.00
C1206C104KARACTU	Kemet	250volts 0.1uF X7R 10%	30000	\$0.056	\$1,680.00
C1812C474KARACTU	Kemet	250volts 0.47uF X7R 10%	18000	\$0.252	\$4,536.00
C1825C105KARACTU	Kemet	250volts 1uF X7R 10%	5000	\$0.648	\$3,240.00
BAV3004WS-7	Diodes Incorporated	Power Switching Diode 200mW 350V	36000	\$0.072	\$2,592.00
ERJ-8ENF1204V	Panasonic	1206 1.2Mohms 1% Tolerance	1000	\$0.01	\$10.00
LTC1799HS5#PBF	Linear Technologies	1kHz to 33MHz Resistor set SOT-23 Oscillator	1000	\$3.04	\$3,040
PCB	Rush PCB		1000	\$1.50	\$1,500
"Arduino" Nano	Variable	USB controlled Microcontroller	1000	\$2.00	\$2,000
571-5103309-1	TE Connectivity	HDR VERT DOUBLE 10P low profile	1000	\$0.627	\$627
				Total (1000)	\$27,226.00
				Total (single)	\$27.23

Questions We Have


- How will PMT load change readings?
- What is the Voltage ripple spec ($\leq 1V$ rms ?)
- What is the dynamic range/stability criterion for anode current?
 - 1% at (10 MHz)(10^5 gain)(10 p.e.) = 2 microAmp ??
- When is the deadline for a design choice
 - Yesterday?

Conclusions

- We have proof-of-principle prototype
 - We think we can improve it to meet spec
- We do not yet have a working PMT base.
 - We think we can get there by April (sooner?)
- Provides a digitally controlled, compact, and efficient alternative to resistive base

Starting Design

Pulse in →

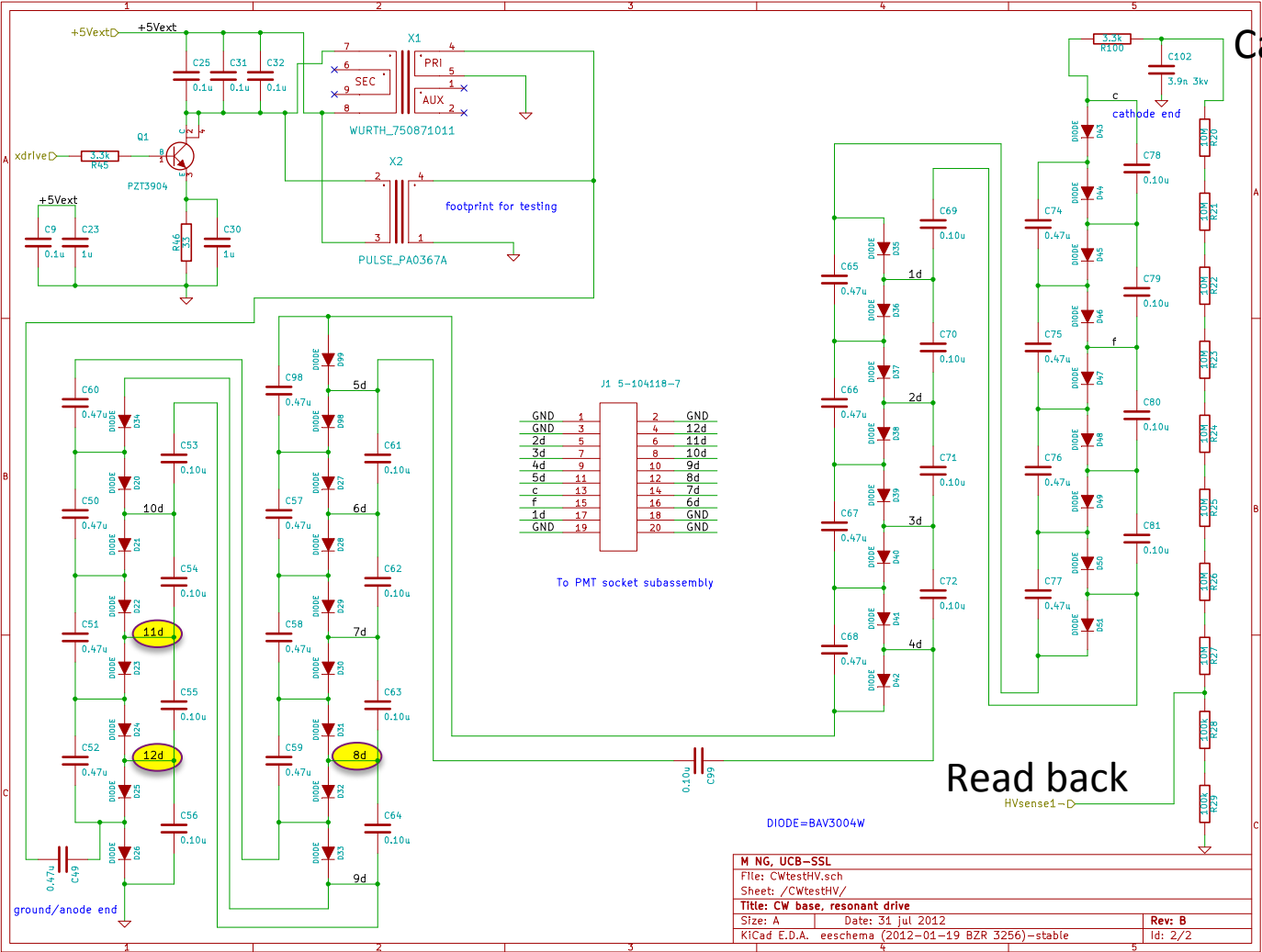

Cathode

Read back

Dynode HV
(12 for AnDY)
10 for NPS

GND	1	2	GND
GND	3	4	12d
GND	5	6	11d
GND	7	8	10d
GND	9	10	9d
GND	11	12	8d
GND	13	14	7d
GND	15	16	6d
GND	17	18	GND
GND	19	20	GND

To PMT socket subassembly

M NG, UCB-SSL		
File: CWtestHV.sch		
Sheet: /CWtestHV/		
Title: CW base, resonant drive		
Size: A	Date: 31 jul 2012	Rev: B
KiCad E.D.A. eeschema (2012-01-19 BZR 3256)-stable		Id: 2/2

Feedback & Set-Point/Readback Communications

Power / I-O

